

Function Specification

This circuit is the Verilog implementation of the toUpper() function for an 8 bit ASCII input character. In the ASCII table, the characters for uppercase A through uppercase Z occupy the values 65–90, and the characters for lowercase a through lowercase z occupy the values 97–122. The difference between any lowercase alphabetical character and its corresponding uppercase character is always 32, or 2^5 . Thus, the fifth bit of the input determines whether the character is uppercase or lowercase. If the fifth bit is 0, it's an uppercase character, and if it's a 1 then its lowercase.

Therefore, to implement the toUpper() function, we must:

1. Detect when the input corresponds to a lowercase letter, which are ASCII values 97-122
2. Set bit 5 to 0 if it is lowercase
3. Leave all other bits unchanged

The function takes inputs 8 bits labeled A0-A7, and outputs 8 bits labeled B0-B7. Since we're only changing the 5th bit, B0, B1, B2, B3, B4, B6, and B7 are all identical to their input.

Circuit Design

Since we do not have the luxury of something as simple as an `if` statement in Verilog, we must create a function to check whether the input is a lowercase letter. Below is the 8 variable k-map for the function L, which returns 1 if the input is a lowercase character and 0 otherwise:

A7A6A5A4A3A2A1A0	0000	0001	0011	0010	0110	0111	0101	0100	1100	1101	1111	1110	1010	1011	1001	1000
0000	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0001	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0011	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
0010	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
0110	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0111	0	0	0	0	0	0	0	0	1	1	1	1	0	1	0	0
0101	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0100	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1100	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1101	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1111	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
1110	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
1010	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
1011	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
1001	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1000	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

In canonical minterm form, this is $L = \sum m(97, 98, 99, \dots, 122)$, or the sum of the 26 minterms representing a-z. Simplifying with the grouping shown above:

- red → $A7A5$
- blue → $A7'A6'A5$
- green → $A7'A6A5A4A3A2$
- orange → $A7'A6A5A4A3A2'A1A0$
- purple → $A7'A5A4'A3'A2'A1'A0'$

We notice that for all groupings, A5 is 1. Thus, the simplified boolean equation is

$$L = A5(A7 + A7'A6' + A7'A6A4A3A2 + A7'A6A4A3A2'A1A0 + A7'A4'A3'A2'A1'A0')$$


Now that we have a way to check if the input is a lowercase letter, we just have to change bit 5 if the input is not a lowercase letter:

$$B5 = A5 * \bar{L}$$


Testbed Implementation

Here is the terminal output and waveforms on gtkwave with an initial input delay of 25 ns:
 
```
PS C:\Users\ \Desktop\softdev\cs211_project1> gtkwave .\toUpper.vcd
GTKWave Analyzer v3.3.100 (w)1999-2019 BSI
[0] start time.
[525000] end time.
```




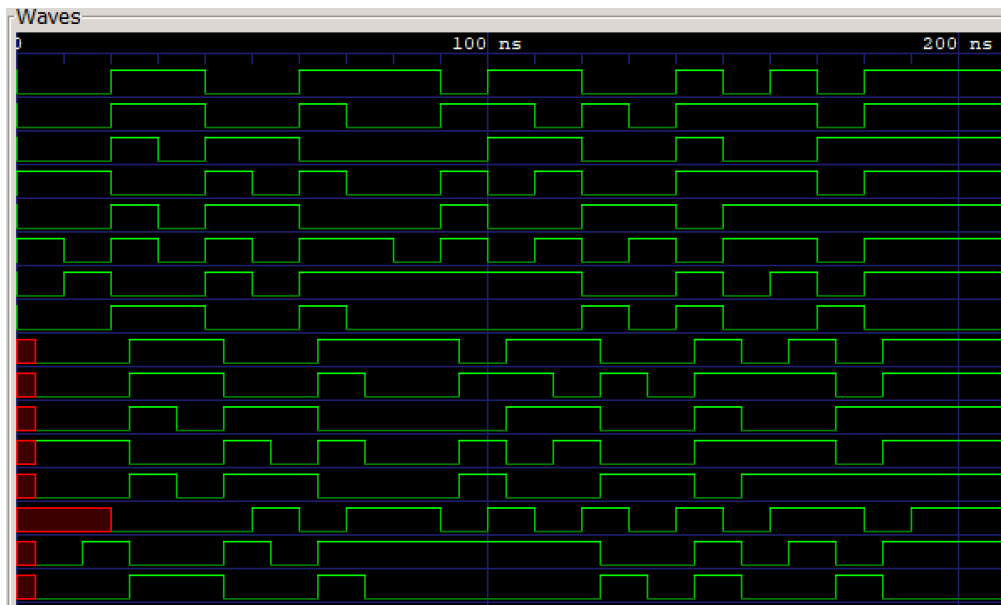Gradually decreasing the input delay by 5 ns each time, the circuit's behavior started to fail at an input delay of 10 ns:



The next input is being fed into the circuit before it finishes processing the current input, leading to irregular output in the B5 bit. Thus, I determined the minimum input delay for the circuit to still function correctly to be ~15 ns, which produces the following terminal output and waveforms:
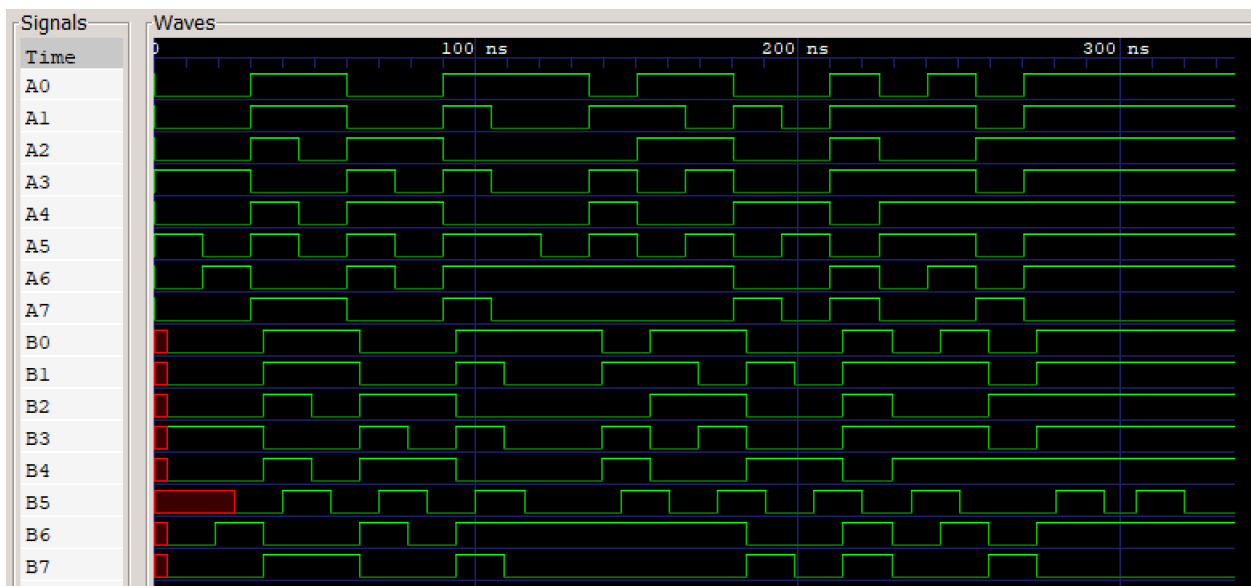
```
PS C:\Users\... \Desktop\softdev\cs211_project1> gtkwave .\toUpper.vcd
GTKWave Analyzer v3.3.100 (w)1999-2019 BSI
[0] start time.
[335000] end time.
```



The input and output are identical for non lowercase letter inputs, and B5 is set to 0 for lowercase letter inputs. The circuit is functioning as expected.