

## Function Specification

This circuit is the Verilog implementation of the toUpper() function for an 8 bit ASCII input character. In the ASCII table, the characters for uppercase A through uppercase Z occupy the values 65–90, and the characters for lowercase a through lowercase z occupy the values 97–122. The difference between any lowercase alphabetical character and its corresponding uppercase character is always 32, or  $2^5$ . Thus, the fifth bit of the input determines whether the character is uppercase or lowercase. If the fifth bit is 0, it's an uppercase character, and if it's a 1 then its lowercase.

Therefore, to implement the toUpper() function, we must:

1. Detect when the input corresponds to a lowercase letter, which are ASCII values 97-122
2. Set bit 5 to 0 if it is lowercase
3. Leave all other bits unchanged

The function takes inputs 8 bits labeled A0-A7, and outputs 8 bits labeled B0-B7. Since we're only changing the 5th bit, B0, B1, B2, B3, B4, B6, and B7 are all identical to their input.

## Circuit Design

Since we do not have the luxury of something as simple as an `if` statement in Verilog, we must create a function to check whether the input is a lowercase letter. Below is the 8 variable k-map for the function L, which returns 1 if the input is a lowercase character and 0 otherwise:

A7A6A5A4A3A2A1A0	0000	0001	0011	0010	0110	0111	0101	0100	1100	1101	1111	1110	1010	1011	1001	1000
0000	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0001	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0011	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
0010	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
0110	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0111	0	0	0	0	0	0	0	0	1	1	1	1	0	1	0	0
0101	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0100	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1100	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1101	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1111	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
1110	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
1010	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
1011	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
1001	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1000	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

In canonical minterm form, this is  $L = \sum m(97, 98, 99, \dots, 122)$ , or the sum of the 26 minterms representing a-z. Simplifying with the grouping shown above:

- red →  $A7A5$
- blue →  $A7'A6'A5$
- green →  $A7'A6A5A4A3A2$
- orange →  $A7'A6A5A4A3A2'A1A0$
- purple →  $A7'A5A4'A3'A2'A1'A0'$

We notice that for all groupings, A5 is 1. Thus, the simplified boolean equation is

$$L = A5(A7 + A7'A6' + A7'A6A4A3A2 + A7'A6A4A3A2'A1A0 + A7'A4'A3'A2'A1'A0')$$

Now that we have a way to check if the input is a lowercase letter, we just have to change bit 5 if the input is not a lowercase letter:

$$B5 = A5 * \bar{L}$$

## Testbed Implementation


Here is the terminal output and waveforms on gtkwave with an initial input delay of 50 ns:

```
PS C:\Users\aslam\Desktop\softdev\cs211_project1> iverilog -o toUpper.vvp toUpper.v toUpper_tb.v
PS C:\Users\aslam\Desktop\softdev\cs211_project1> vvp .\toUpper.vvp
VCD info: dumpfile toUpper.vcd opened for output.

RESULT: 19 passed, 0 failed
toUpper_tb.v:60: $finish called at 950000 (1ps)
PS C:\Users\aslam\Desktop\softdev\cs211_project1> gtkwave .\toUpper.vcd

GTKWave Analyzer v3.3.100 (w)1999-2019 BSI

[0] start time.
[950000] end time.
```

 

Gradually decreasing the input delay, I settled on 26 ns as the minimum for the circuit to function properly.